

# Experiment 5: sequence generator

Narne Avinash Chowdary , Roll Number-200070047

EE-214 WEL, IIT Bombay

October 2, 2021

Overview of the experiment:

## Sequence generator :

In this experiment we have to generate the given sequence shown in fig1 by using flipflops and inputs as clock and reset outputs are 3 bit number.

 


Figure 1: Sequence generator

- > In this lab we have to do both structural and behavioral models .
- > In structural model we have to do port maps for flipflops and also we have to define functions for flip flop inputs in terms of signals
- > Whereas in behavioral one we can directly write by using case and if function.

Approach to the Experiment:

**Structural:**

Firstly we have to write vhdl code for two different flipflops because when reset = 1 then it should go to 010 so first and third flipflops are same , middle one is different .

Now we should write functions for D1,D2,D3,D4 in terms of Q1,Q2,Q3,Q4

After solving the K-maps we got them as follows :

$$D2 = Q0 \text{ xnor } (Q1 \text{ xor } Q0)$$

$$D1 = Q2 \cdot (\text{not } Q0) + (\text{not } Q2) \cdot (\text{not } Q1)$$

$$D0 = (\text{not } Q2) \cdot Q0 + Q2 \cdot Q1$$

So we have to write behavioral equations for this and port map to flip flops

 
**2.3 Circuit Diagram:**

Figure 2: Circuit diagram of the sequence generator

**Behavioral :**

Here no need of port mapping we can directly write when s\_2 then s\_0 like that and reset should go to 010 . Here we use if and case function to design the sequence.

Design document and VHDL code:

Structural:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
library work;
```

```
use work.flipflops.all;
```

```
entity sequence_generator_structural is
```

```
port (reset,clock: in std_logic;
```

```
y:out std_logic_vector(2 downto 0));
```

```
end entity sequence_generator_structural;
```

architecture struct of sequence\_generator\_structural is

signal D2,D1,D0 :std\_logic;

signal Q:std\_logic\_vector(2 downto 0);

begin

-- write the equations here

D2<=(Q(2) xnor (Q(1) xor Q(0)));

D1<=((Q(2) and (not Q(0))) or ((not Q(2)) and (not Q(1))));

D0<= ((Q(0) and (not Q(2))) or (Q(2) and Q(1)));

y(2)<=Q(2);

y(1)<= Q(1);

y(0)<=Q(0);

-- Do the port mapping

--asynchronous reset

--Q0

dff\_0 : dff2 port map(D0,clock,reset,Q(0));

--Q1

dff\_1 : dff1 port map(D1,clock,reset,Q(1));

--Q2

dff\_2 : dff2 port map(D2,clock,reset,Q(2));

end struct;

Behavioral:

```
library ieee;
```

```
use ieee.std_logic_1164.all;
```

```
entity sequence_behavior is
```

```
port (reset,clock: in std_logic;
```

```
      y:out std_logic_vector(2 downto 0));
```

```
end entity sequence_behavior ;
```

```
architecture behav of sequence_behavior is
```

```
--state binary encoding
```

```
signal state:std_logic_vector(2 downto 0);
```

```
constant s_2:std_logic_vector(2 downto 0):="010";
```

```
constant s_0:std_logic_vector(2 downto 0):="000";
```

```
constant s_1:std_logic_vector(2 downto 0):="001";
```

```
constant s_3:std_logic_vector(2 downto 0):="011";
```

```
constant s_4:std_logic_vector(2 downto 0):="100";
```

```
constant s_5:std_logic_vector(2 downto 0):="101";
```

```
constant s_6:std_logic_vector(2 downto 0):="110";
```

```
constant s_7:std_logic_vector(2 downto 0):="111";
```

```
--write the remaining constant declarations
```

```
begin
```

```
-- process for next state and output logic
```

```
reg_process: process(clock,reset)
```

```
begin
if(reset='1')then
state<=s_2; -- write the reset state
elsif(clock'event and clock='1')then
case state is
    --reset
    when s_2=>
state<=s_0;

        when s_1=>
state<=s_3;
    when s_3=>
state<=s_5;
    when s_4=>
state<=s_2;
    when s_5=>
state<=s_4;
    when s_6=>
state<=s_7;
    when s_7=>
state<=s_1;
    when s_0=>
state<=s_6;
    -- write the remaining choices
```

--DEFAULT CASE

when others=>

state<="010";-- write the reset state

end case;

end if;

end process reg\_process;


-- output logic concurrent statemet or one more process

y<=state;


end behav;

RTL VIEW:

Structural:

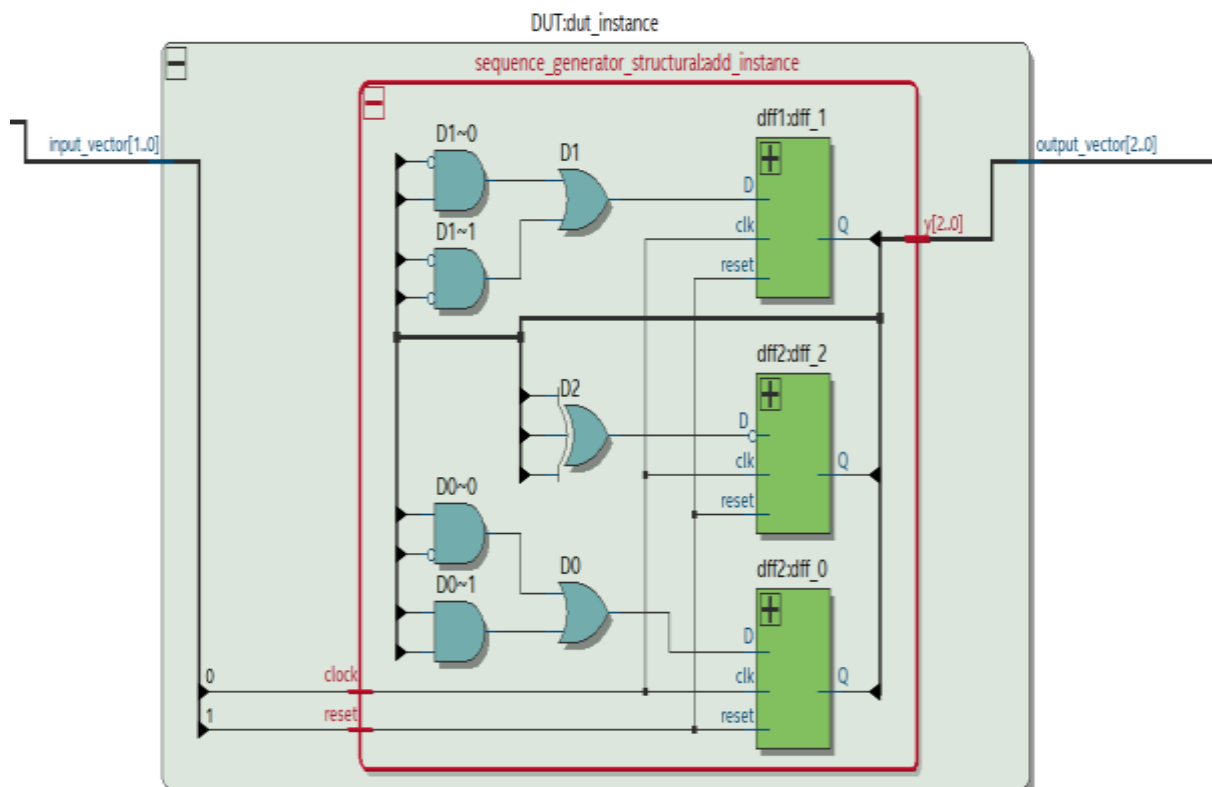

Behavioral:

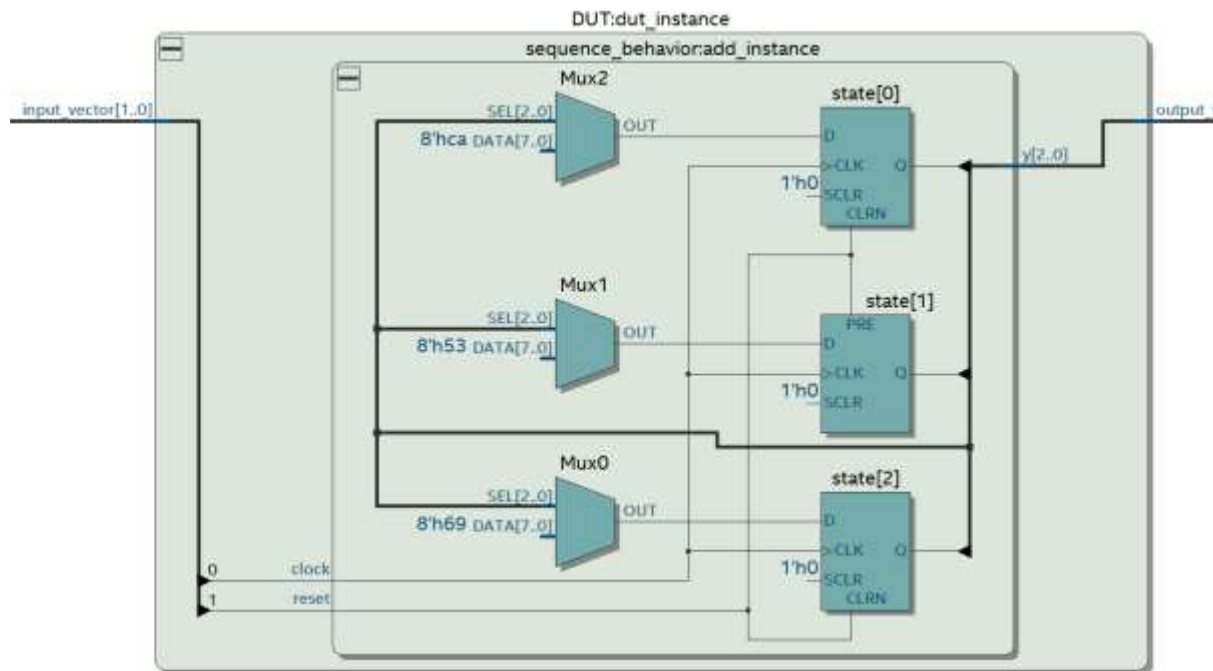

DUT Input/Output Format:

reset => input\_vector(1),


clock=> input\_vector(0),

y(2)=>output\_vector(2),

y(1)=>output\_vector(1),


y(0)=>output\_vector(0)

RTL SIMULATION:

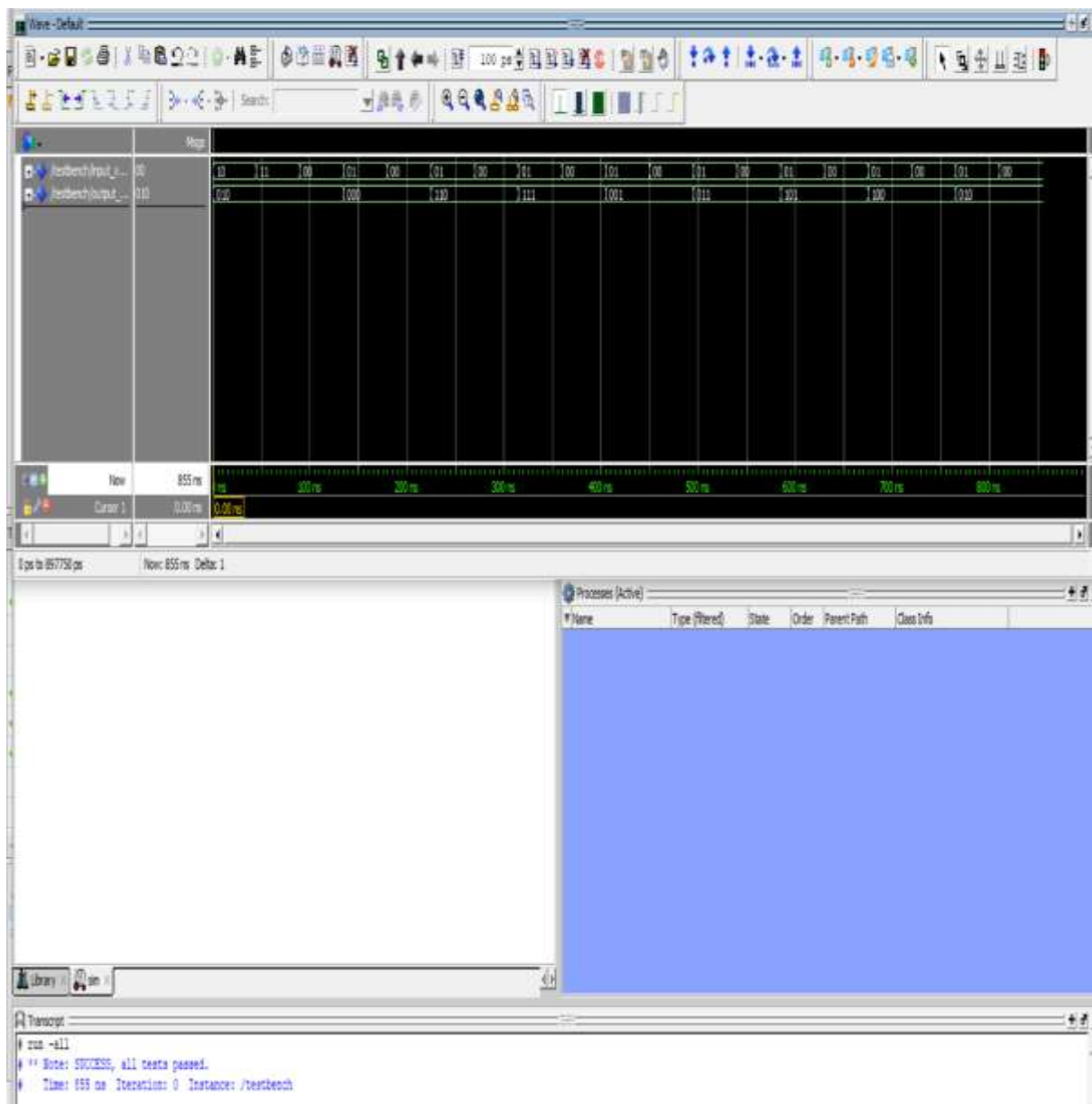

Gate – Level Simulation:



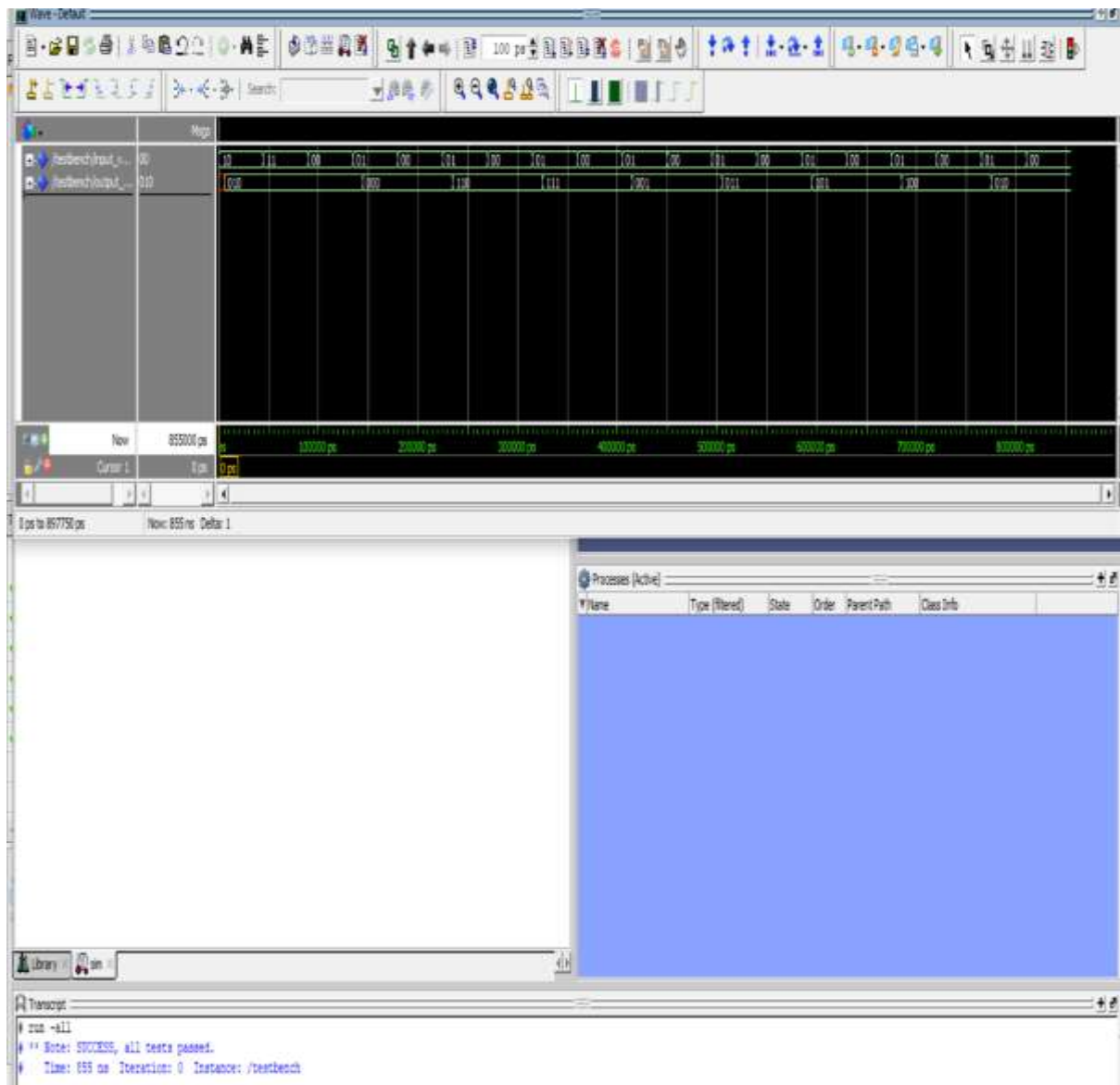

## Krypton Board:

After completion of simulation on Quartus, the sequence generator is implemented on Krypton board using UrJTAG. Later we verify this using ScanChain and ideal values that Krypton board implement to this circuit. We confirm whether the design is correctly implemented while implementing UrJTAG and the svf file obtained.

## Observations:

It is observed that design is correct and it is successfully verified using ScanChain by viewing the TRACEFILE cases in the out.txt file generated in project directory.

Below are some of the cases in out.txt file.

---

10	010	Success
11	010	Success
00	010	Success
01	000	Success
00	000	Success
01	110	Success
00	110	Success
01	111	Success
00	111	Success
01	001	Success
00	001	Success
01	011	Success
00	011	Success
01	101	Success
00	101	Success
01	100	Success
00	100	Success
01	010	Success
00	010	Success